
 


Latch and Flip-Flop roundup...


Standard RS Latch

 

R	S	Q	\overline{Q}
1	0	0	1
0	1	1	0
0	0	Q	\overline{Q}
1	1	1	1 – not valid!




Latch and Flip-Flop roundup...

 


Clocked RS Latch

Output can only change when
CLK=1

 


Latch and Flip-Flop roundup...

 

Edge-triggered R-S Flip-flop

Can only change output state during
the transition from CLK=1 to CLK=0

Latch and Flip-Flop roundup...

 


K	J	Q
0	0	Q
0	1	1
1	0	\overline{Q}
1	1	\overline{Q}

Standard J-K Flip Flip

Only one of the inputs to the R-S latch can be 1 at any given time, thus the invalid R=1, S=1 condition is resolved

Latch and Flip-Flop roundup...

 


D	Q
1	1
0	0

D (data) Flip Flop

When CLK=1 data in the
D line is reflected by Q,
remains stored after CLK=0
regardless of D


Latch and Flip-Flop roundup...

 

T (toggle) Flip Flop

Just a J-K with both inputs set to 1,
Output changes state at each clock pulse

 Registers: Storing more than 1 bit of data




4 bit parallel-load register

Data is loaded on the clock pulse


You know already what to do if you want, say, 2 of these, or 4 of these, or 8 of these: i.e. you can build memory blocks!

 Registers: Storing more than 1 bit of data



4 bit shift register
Data shifts to the 'left' (in binary terms)
on each clock pulse

Simple counter

 

4 bit ripple counter
Counts the number of pulses
In CLK

Each individual output works
also as a frequency divider for CLK