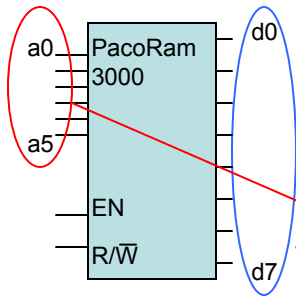


Designing a memory bank



- Suppose we're working with this chip
- What is the memory capacity?
 - First, look at the number of address lines
 - 6 address lines implies $2^6=64$ addresses in the chip
 - Now look at the number of data lines
 - 8 data lines implies 8 bits (1 byte) per address
 - Hence, this chip can hold 64 bytes of memory
 - Typically the chip will be labeled 64 x 8, meaning 64 addresses, 8 bits per address.

Problem:

Design a memory bank with 256 bytes of memory using the PacoRam3000 chips and decoders

- First question: How many memory chips we need?


$$4 - 64 \text{ bytes} * 4 = 256 \text{ bytes}$$

- What type of decoder will we use?


A 2 to 4 decoder, 2 selection lines, 4 output lines

Memory bank design

1 – Hook up the data bus

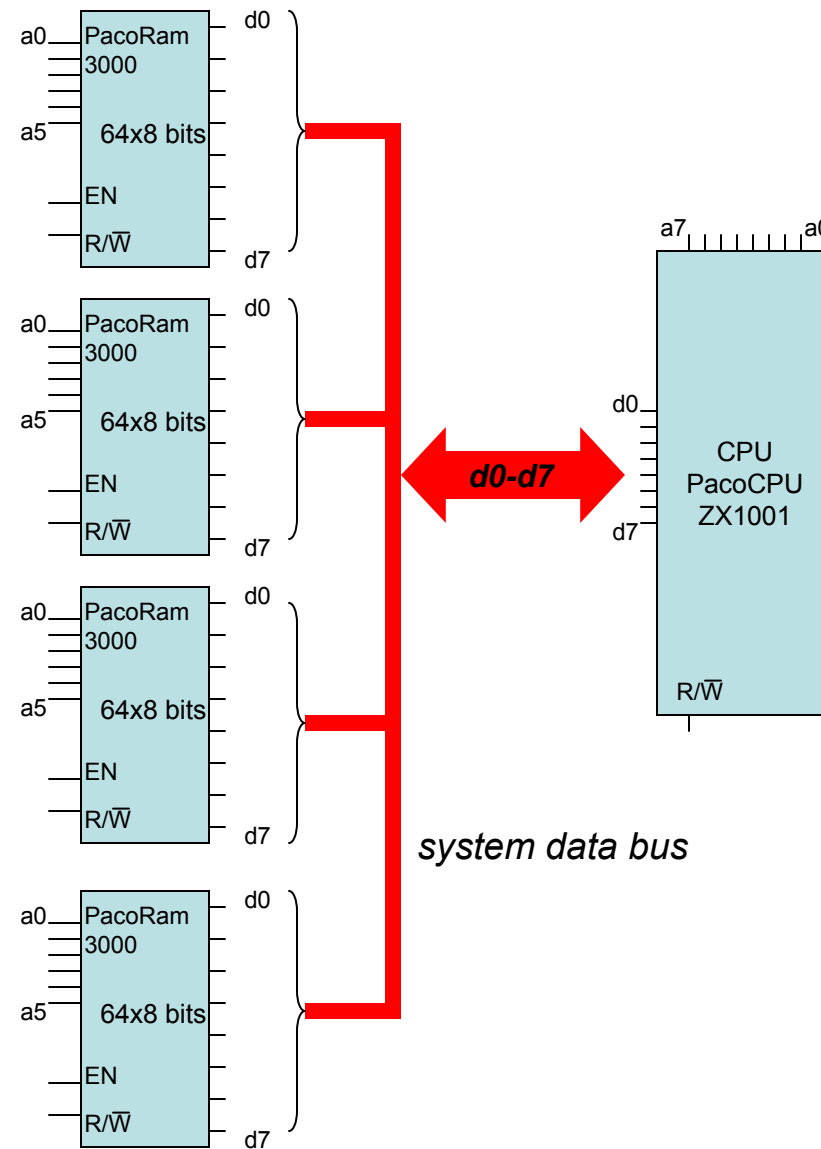


Memory bank design

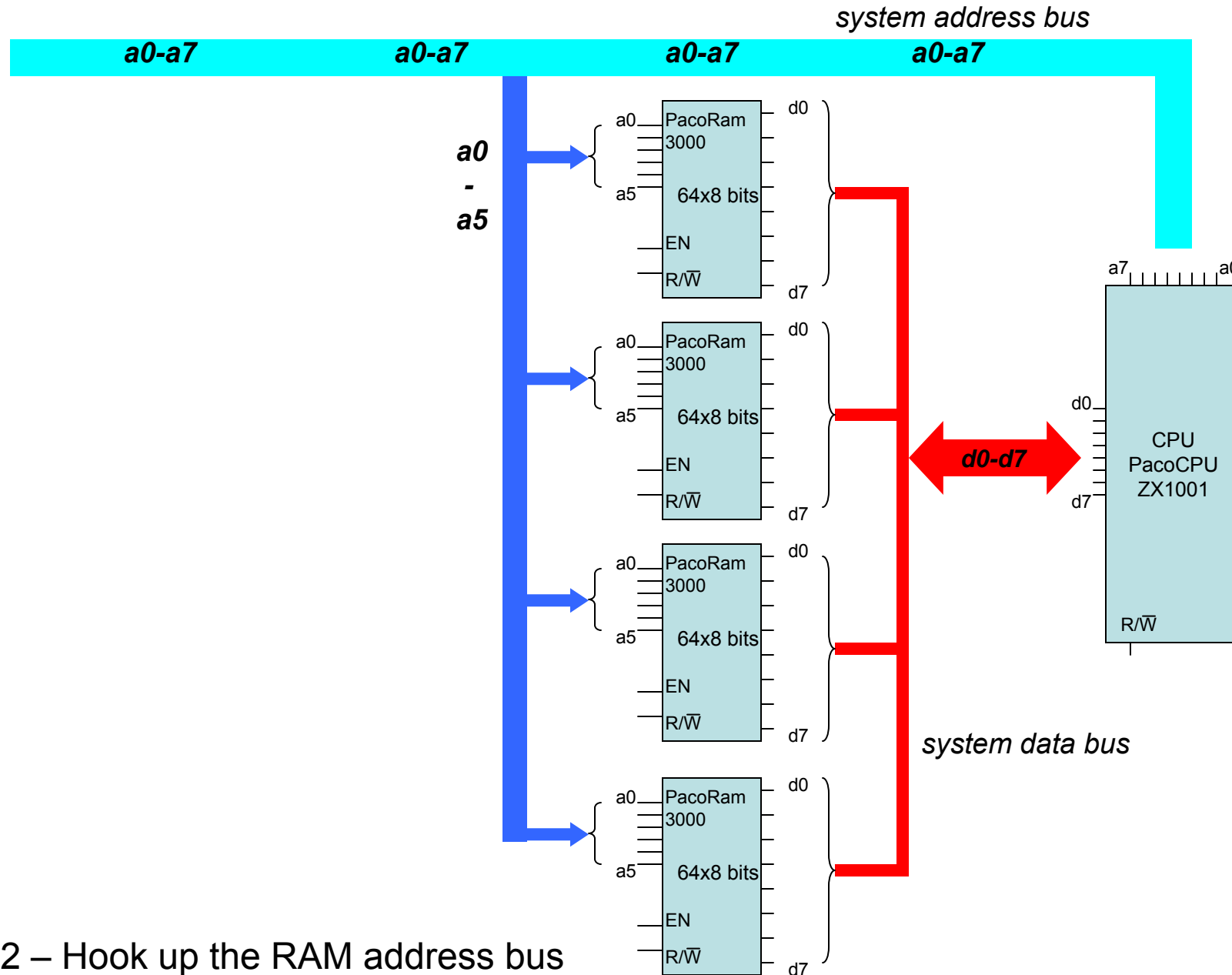


2 – Hook up the RAM address bus


Memory bank design

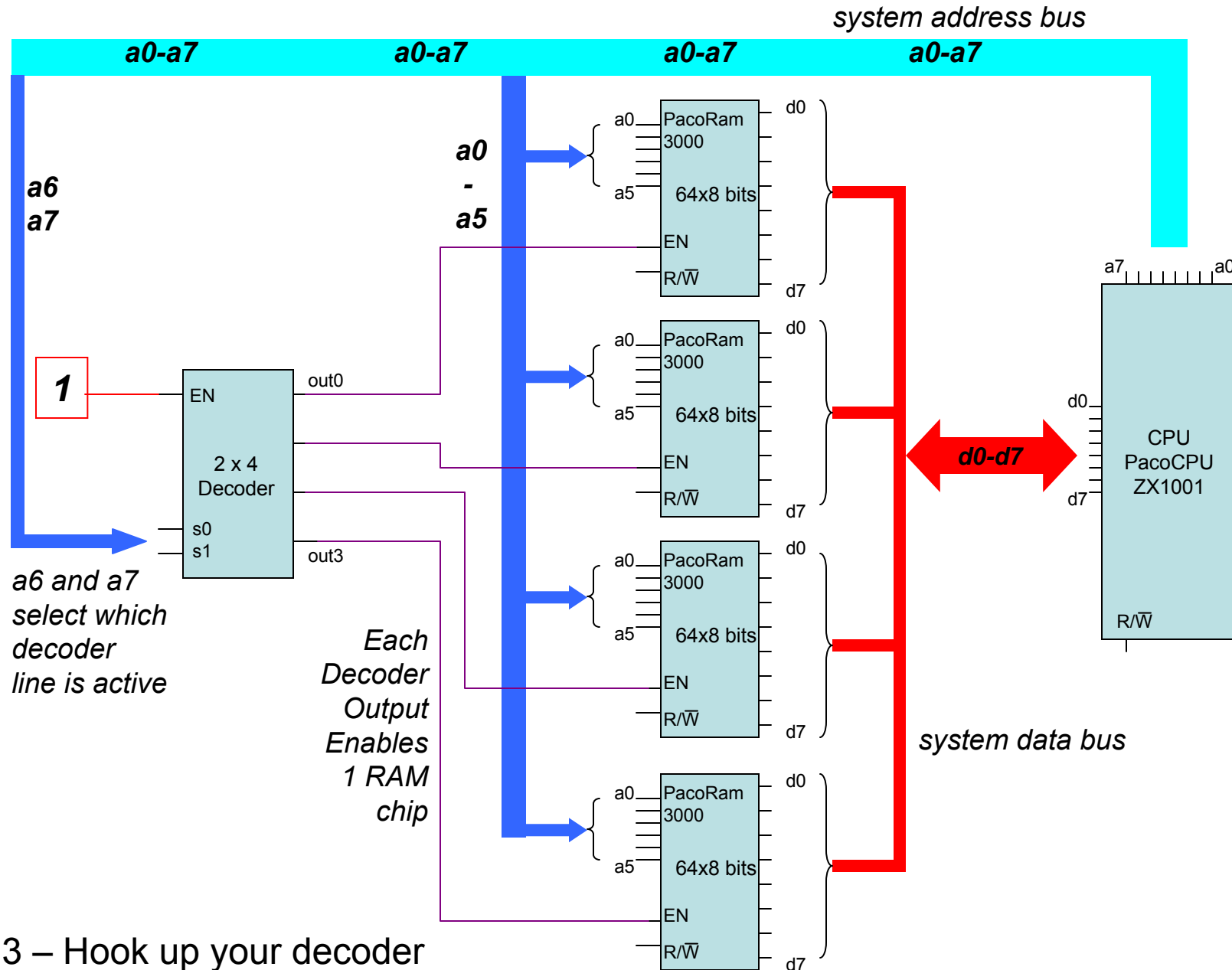


Memory bank design

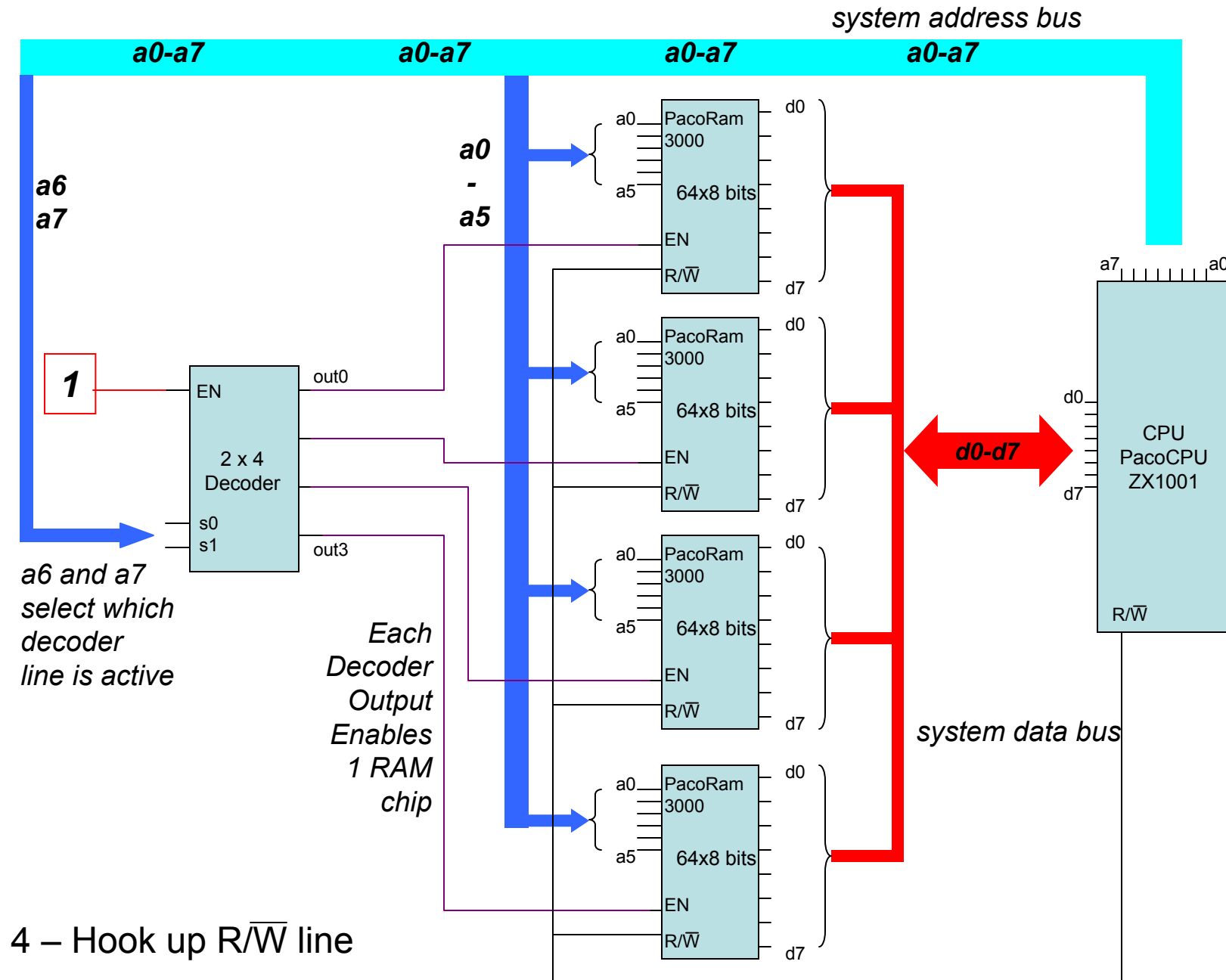


Memory bank operation

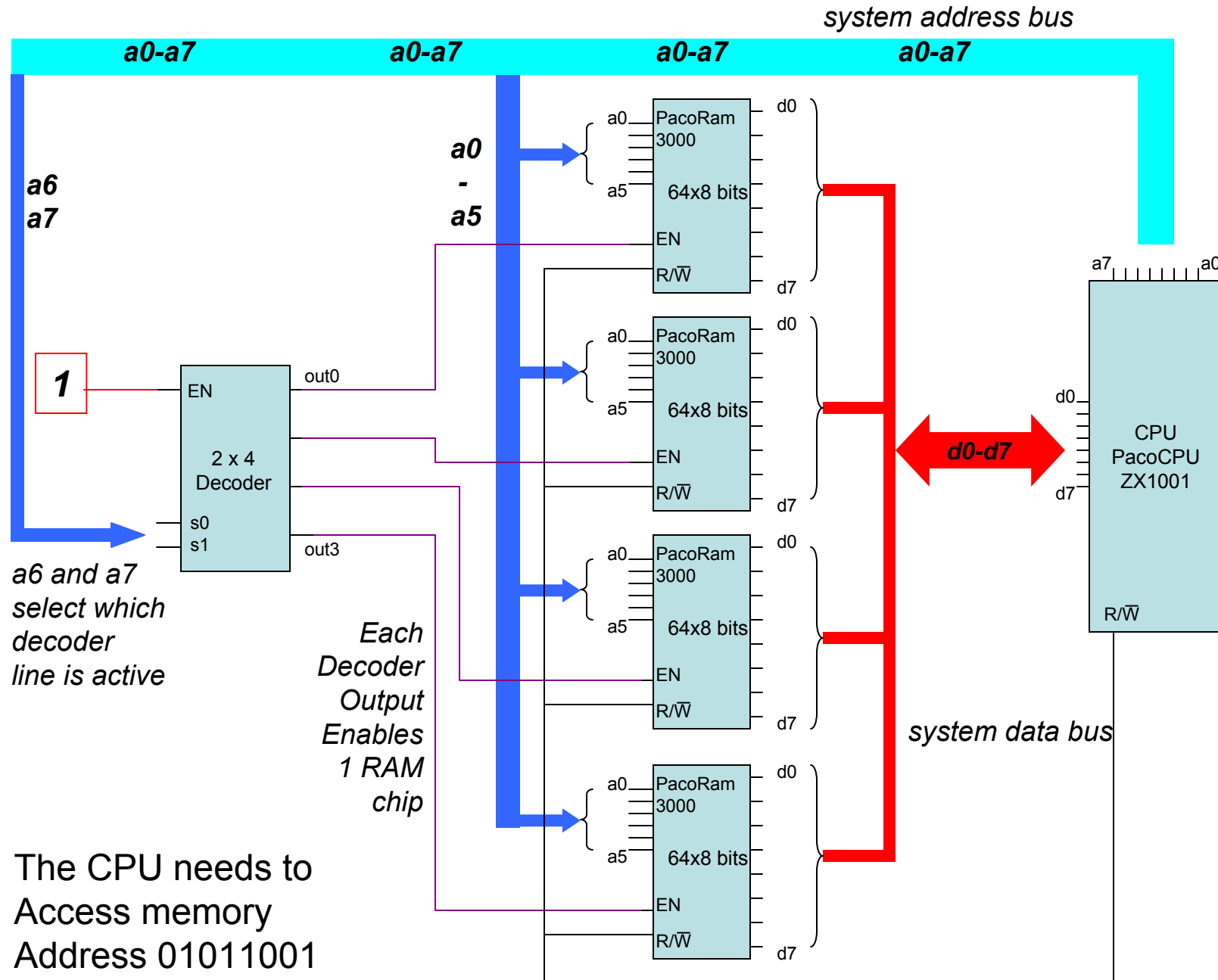


Memory bank operation

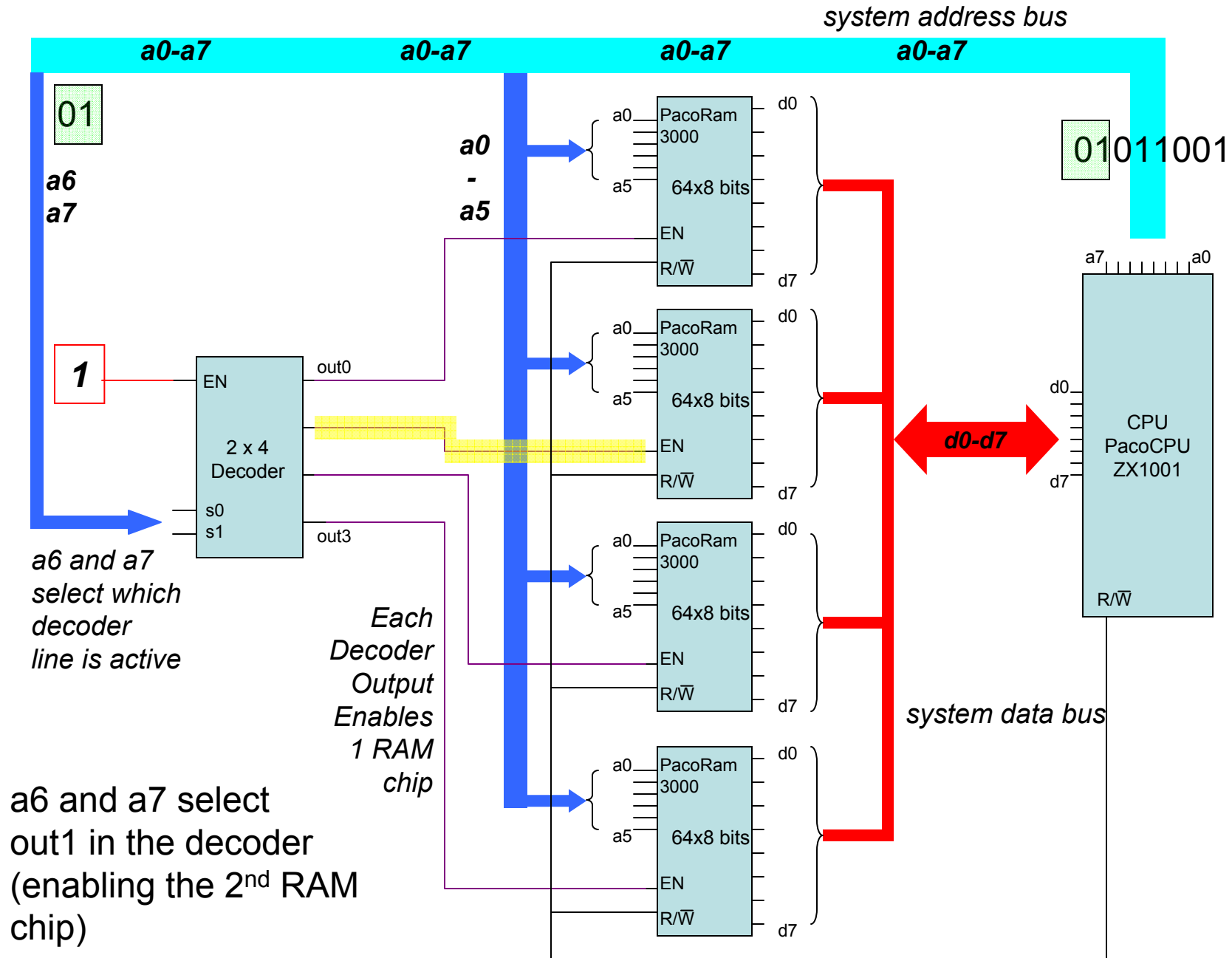



Memory bank operation

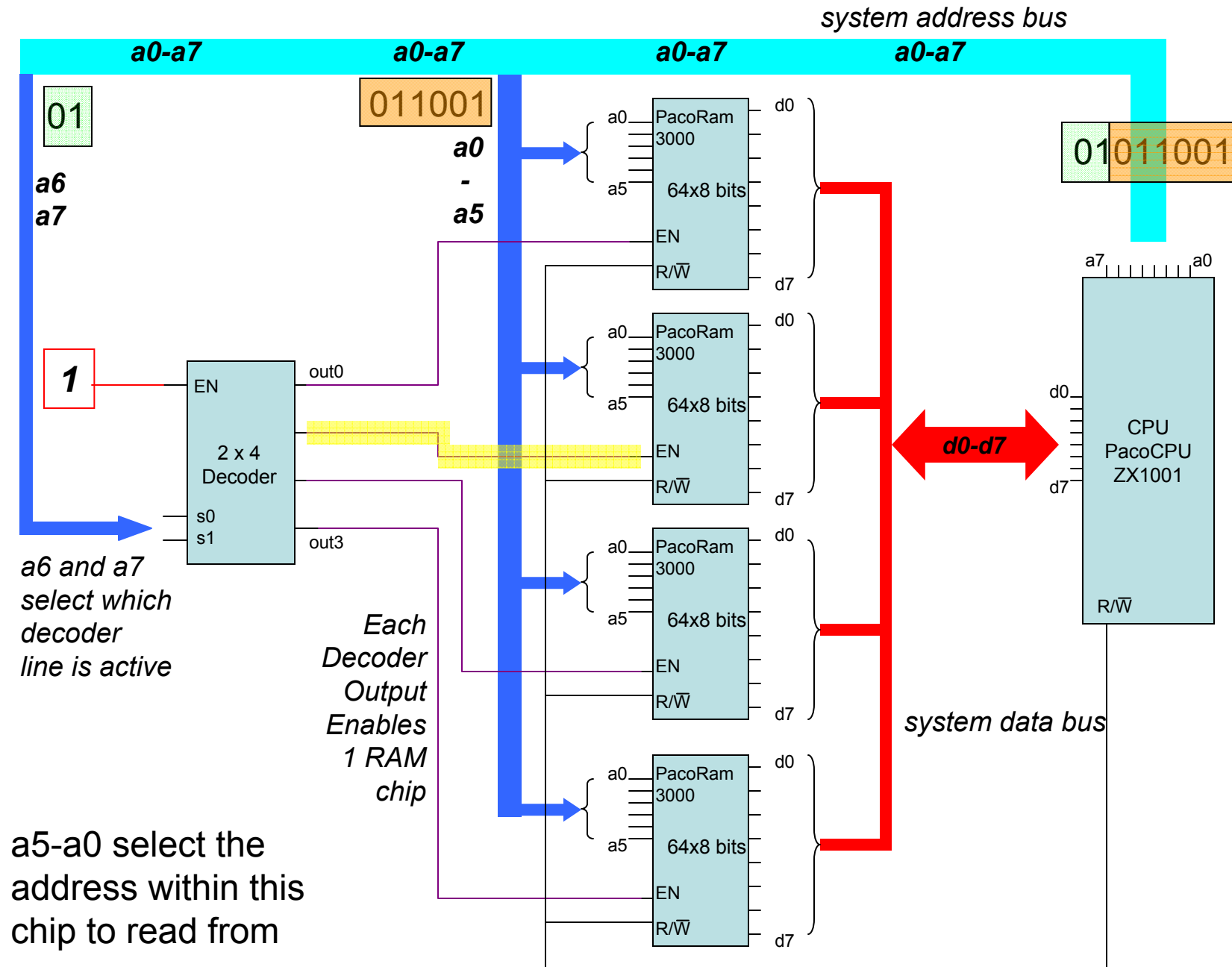

Memory bank operation

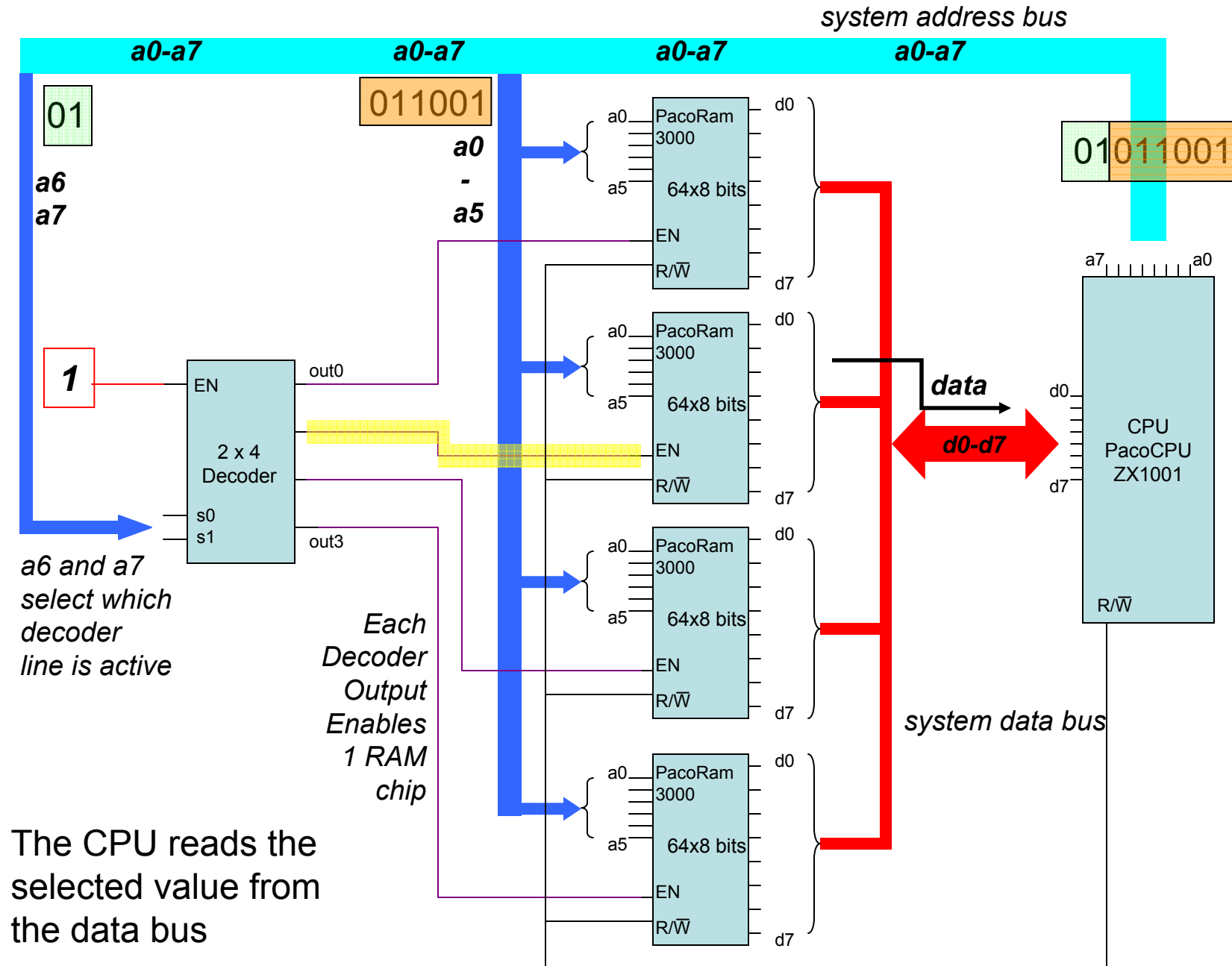

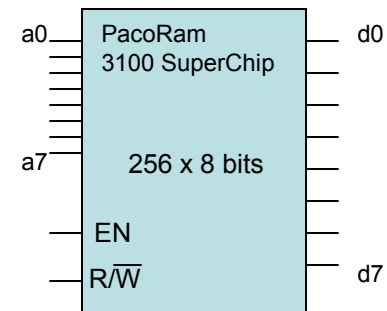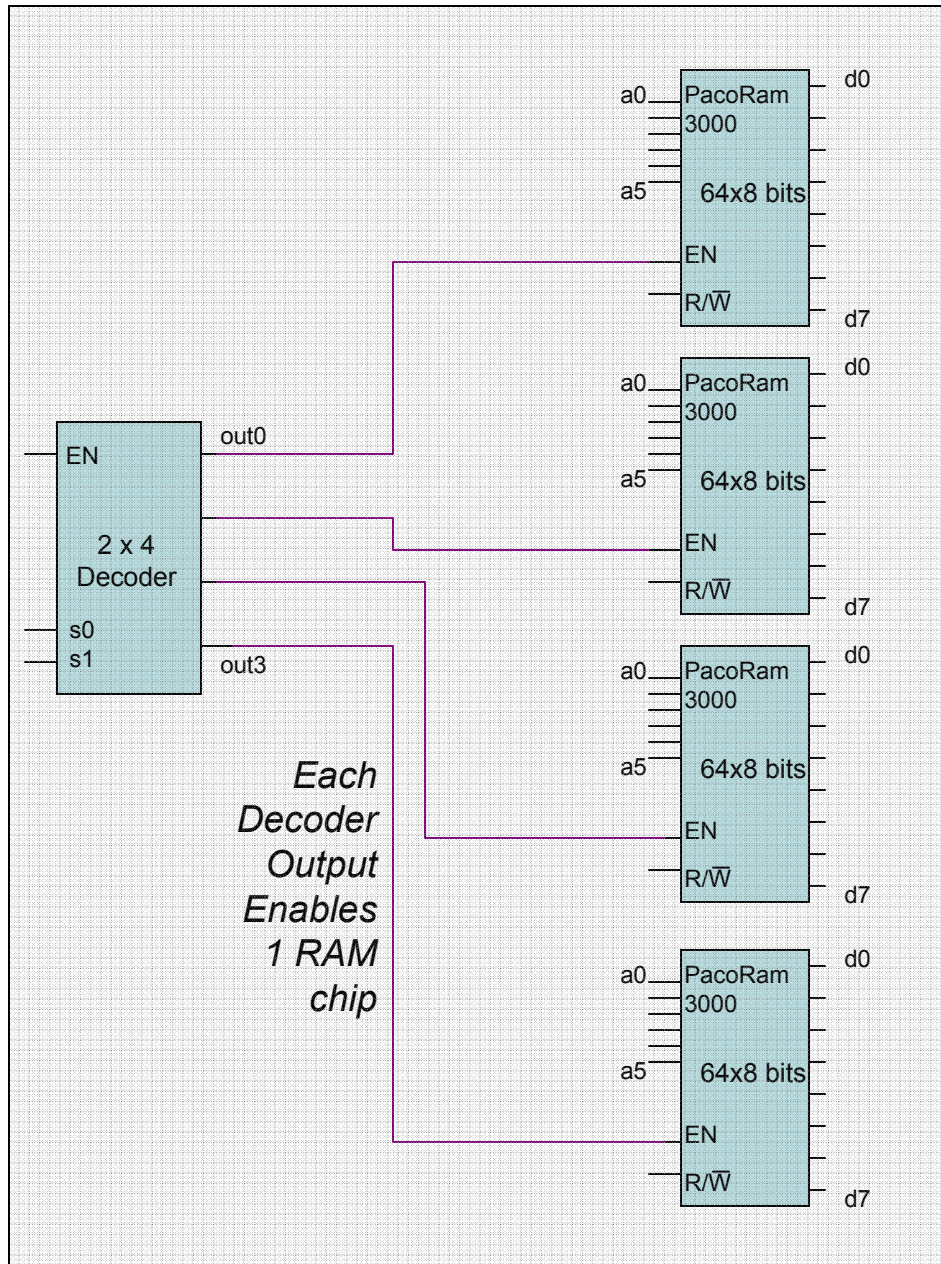Memory bank – expanding with more decoders



As long as I have available address lines, I can keep adding more memory